

# Sample Test: Aptitude Test "Elektrotechnik" - MRBE

## Instructions

Answer all questions.

## Part A: Multiple Choice (2 points each)

1. **Problem.** Which law states that the algebraic sum of currents at any node of an electric circuit is zero?


- (a) Ohm's Law
- (b) Kirchhoff's Voltage Law
- (c) Kirchhoff's Current Law
- (d) Tellegen's Theorem

**Answer: (c) Kirchhoff's Current Law (KCL).** states that  $\sum I_{\text{in}} = \sum I_{\text{out}}$ , i.e., the net current into a node of an electric circuit is zero.

2. **Problem.** In a DC circuit, the maximum power is transferred to a resistive load when:

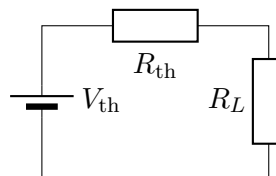- (a) The load resistance is null.
- (b) The load resistance equals the source Thévenin equivalent resistance.
- (c) The load resistance is infinite.
- (d) The source voltage equals the load voltage.

**Answer: (b)** For a linear source with Thévenin resistance  $R_{\text{th}}$ , the maximum power transferred to the load occurs when  $R_L = R_{\text{th}}$ . See proof below.



- i. The current through the load is

$$I = \frac{V_{\text{th}}}{R_{\text{th}} + R_L}.$$

- ii. The corresponding power transferred to the load is

$$P_L = I^2 R_L = \left( \frac{V_{\text{th}}}{R_{\text{th}} + R_L} \right)^2 R_L = \frac{V_{\text{th}}^2 R_L}{(R_{\text{th}} + R_L)^2}.$$

iii. Now we need to maximize  $P_L$  with respect to  $R_L$ , i.e., differentiate its function.

$$f(R_L) = \frac{V_{th}^2 R_L}{(R_{th} + R_L)^2}.$$

The first derivative is

$$\frac{df}{dR_L} = V_{th}^2 \cdot \frac{(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L)}{(R_{th} + R_L)^4},$$

and, when we simplify its denominator, we find

$$(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L) = (R_{th} + R_L)(R_{th} - R_L).$$

Thus,

$$\frac{df}{dR_L} \propto (R_{th} - R_L).$$

iv. Now we can set the derivative to zero, finding

$$R_{th} - R_L = 0 \implies R_L = R_{th}.$$

v. A second derivative test will tell us if the power is positive or negative. We will find that it is negative at  $R_L = R_{th}$ , so the power is maximum.

3. **Problem.** Which of the following is *not* a correct assumption for an ideal operational amplifier?

- (a) Its input impedance is infinite.
- (b) It has a zero output impedance.
- (c) Its bandwidth is infinite.
- (d) It has a finite open-loop gain.

**Answer: (d)** An ideal op-amp presents an *infinite* open-loop gain (not *finite*), infinite input impedance, zero output impedance, and infinite bandwidth.

4. **Problem.** The power factor of a linear purely capacitive circuit is:

- (a) 1.
- (b) 1/2.
- (c) Leading.
- (d) Lagging.

**Answer: (c) Leading.** For a pure capacitor, its current leads its terminal voltage by  $90^\circ$ . The magnitude of  $\cos \varphi$ , i.e. its power factor, is 0, and the sign (lead/lag) is *leading*.

5. **Problem.** Which of the following implements a *first-order low-pass* filter response? Assume the output is taken across the indicated element.

- (a) Series RL, output across  $L$ .
- (b) Series RC, output across  $C$ .
- (c) Parallel LC in a lossless circuit.

(d) Series RC, output across  $R$ .

**Answer: (b)** A series RC with the output across the capacitor is a first-order low-pass filter. We can think that at low frequency the capacitor impedance is high, so that higher voltages appear across  $C$ , while at high frequency the capacitor impedance is low and its voltage drops.

## Part B: Short Answer (3 points each)

6. **Problem.** Explain the difference between *active*, *reactive*, and *apparent* power in AC linear circuits.

**Answer:** Active power  $P$  (watts) is the real power dissipated or converted to work/heat. In a single-phase circuit,  $P = VI \cos \varphi$ , where  $V$  is the RMS value of the voltage,  $I$  is the RMS value of the current, and  $\cos \varphi$  is the angle representing the displacement between the sinusoidal voltage and current. Reactive power  $Q$  (vars) is the power that oscillates between the circuit elements. In a single-phase circuit,  $Q = VI \sin \varphi$ . Apparent power  $S$  (VA) is the product  $S = VI$  and satisfies  $S^2 = P^2 + Q^2$ ; the power factor is  $PF = \cos \varphi = P/S$ .

7. **Problem.** State Thévenin's theorem and describe its practical application.


**Answer: Thévenin's theorem:** Any linear, bilateral two-terminal network can be replaced by an equivalent voltage source  $V_{th}$  in series with a resistance  $R_{th}$  as seen from the terminals. **Application:** This theorem simplifies load analysis and design, e.g., selecting  $R_L$  for maximum power transfer. Example: Compute  $V_{th}$  as the open-circuit terminal voltage; compute  $R_{th}$  by turning off independent sources (i.e., voltage sources are shorted, and current sources are open circuits) and finding the equivalent resistance.

8. **Problem.** Draw a simplified equivalent circuit of a DC machine without its excitation windings and label its main components. Afterwards, calculate the average power at the machine shaft, neglecting any mechanical losses and assuming steady state conditions.

**Answer:** A simple armature circuit of a separately excited field machine includes the source voltage  $V_a$ , the machine series armature resistance  $R_a$ , its inductance  $L_a$ , and its back-EMF source  $E = K\phi\omega$  opposing the applied voltage. The electrical dynamics are then defined by the differential equation

$$V_a = E + i_a R_a + L_a \frac{di_a}{dt}, \quad E = K\phi\omega,$$

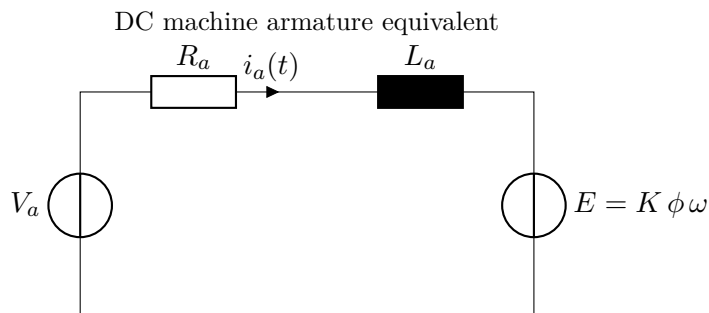and the electromechanical torque is  $T = K\phi i_a$ .



The average power developed at the machine shaft is given by

$$P = E \times i_a,$$

where

$$i_a = \frac{V_a - E}{R_a}.$$

Thus,

$$P = \frac{V_a E - E^2}{R_a}.$$

9. **Problem.** Define the quality factor  $Q$  in a linear RLC series circuit and explain its significance to analog filter design.


**Answer:** For a series RLC at resonance  $\omega_0$ ,

$$Q = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}.$$

Higher  $Q$  implies a sharper resonance, i.e., a narrower filter bandwidth  $B = \omega_0/Q$ , higher selectivity, and larger peak reactive currents or voltages for a given source.

10. **Problem.** Draw an equivalent electrical circuit of a two-winding transformer referred to its primary side, depicting the magnetizing inductance, the leakage inductances, core losses, and winding losses. What is the role of *magnetizing inductance* in a transformer?

**Answer:**

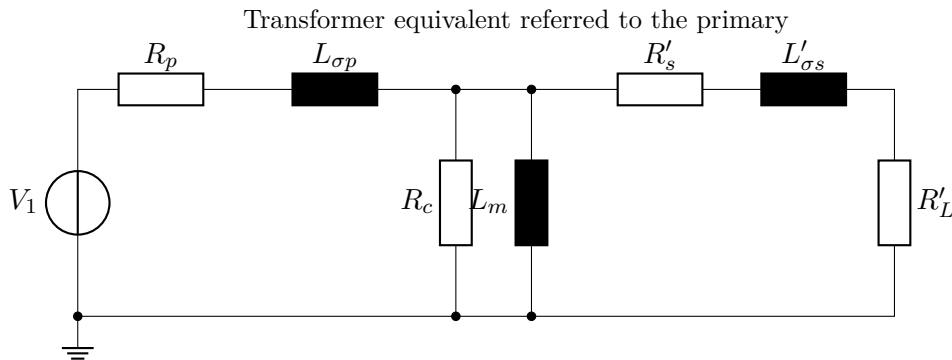

The magnetizing inductance  $L_m$  models the current needed to establish the mutual magnetic flux in the core. It primarily determines the no-load current and influences voltage regulation and core excitation. In the equivalent circuit,  $L_m$  appears as a shunt branch (usually on the primary side) in parallel with core-loss resistance.

## Part C: Problem Solving (4 points each)

11. **Problem.** A copper wire is 15 m long and has a diameter 1.5 mm. Compute its total electric resistance using a resistivity of  $\rho_{Cu} = 1.68 \times 10^{-8} \Omega \text{ m}$ .

**Answer:** The wire radius is  $r = 0.75 \text{ mm} = 7.5 \times 10^{-4} \text{ m}$  and its cross-sectional area

$$A = \pi r^2 = \pi(7.5 \times 10^{-4})^2 = 1.767 \times 10^{-6} \text{ m}^2.$$

Thus, the resistance is found with

$$R = \rho \frac{L}{A} = \frac{1.68 \times 10^{-8} \times 15}{1.767 \times 10^{-6}} \approx 0.143 \Omega.$$

12. **Problem.** For a series RLC with  $L = 0.1 \text{ H}$  and  $C = 100 \mu\text{F}$ , compute the resonant frequency  $f_0$  of the circuit.

**Answer:**

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 100 \times 10^{-6}}} = \frac{1}{2\pi\sqrt{10^{-5}}} \approx 50.3 \text{ Hz}.$$

13. **Problem.** A non-inverting amplifier uses  $R_1 = 10\text{ k}\Omega$  connected to ground, and  $R_2 = 30\text{ k}\Omega$  as a feedback resistor. What is the voltage gain of this amplifier?

**Answer:** For a non-inverting amplifier:

$$A_v = 1 + \frac{R_2}{R_1} = 1 + \frac{30\text{ k}\Omega}{10\text{ k}\Omega} = 4.$$

14. **Problem.** A transformer has a primary side voltage with an RMS value of 400 V. Its turns ratio is  $N_p : N_s = 8 : 1$ . Find the secondary side RMS voltage value.

**Answer:**

$$V_s = V_p \frac{N_s}{N_p} = 400\text{ V} \times \frac{1}{8} = 50\text{ V}.$$

15. **Problem.** A DC machine draws 10 A at 220 V and delivers 2 kW mechanical output. Calculate its efficiency.

**Answer:** Its input power is given by

$$P_{\text{in}} = VI = 220 \times 10 = 2200\text{ W}.$$

The output power is  $P_{\text{out}} = 2000\text{ W}$ . Thus, the efficiency of this machine is

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\% = \frac{2000}{2200} \times 100\% \approx \boxed{90.9\%}.$$