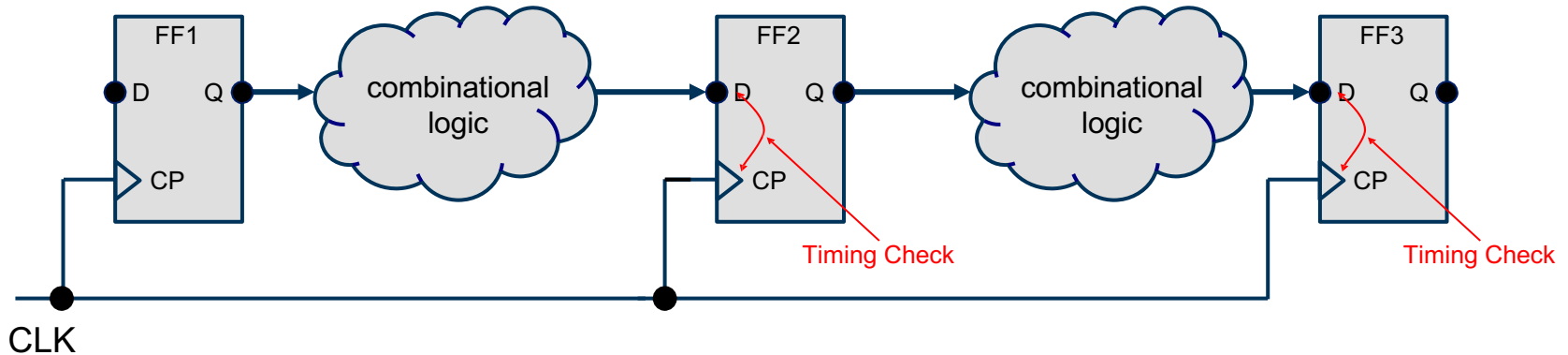


# Back to the Root of Timing

Grace Li Zhang


Chair of Electronic Design Automation

# Digital Circuits




- **Combinational logic blocks** perform computation.
- **Sequential components** such as flip-flops synchronize signal propagation.
- **Timing constraints** should be checked at flip-flops.

# Timing of Digital Circuits

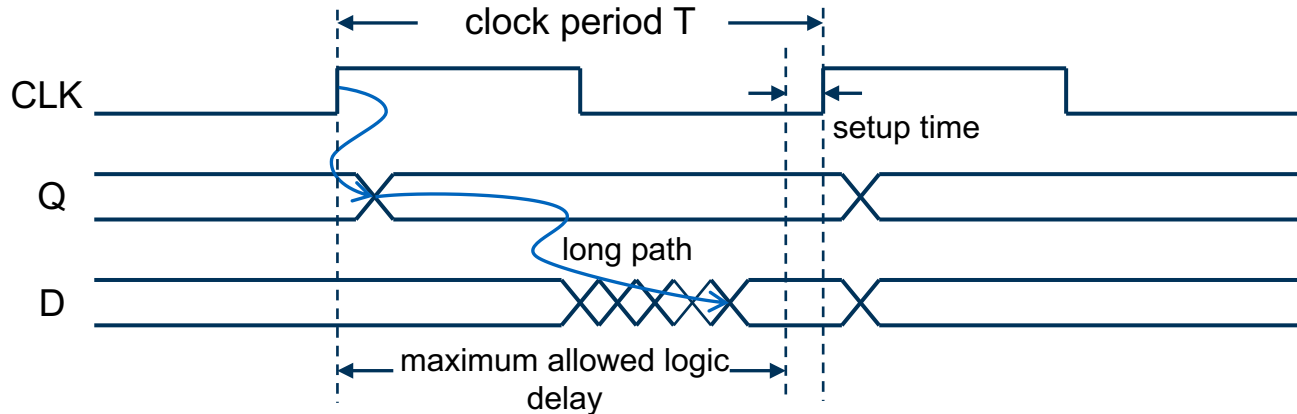

 The delays of the longest paths determine the minimum clock period and thus the maximum clock frequency.



Clock-to-q delay  $t_{cq}$ : 3  
Setup time  $t_{su}$ : 1

$$T_{\min} = t_{cq} + d_{\max} + t_{su} = 3 + 17 + 1 = 21$$

# Clock Frequencies: ITRS 2004 and 2013

## ITRS (International Technology Roadmap for Semiconductors) 2004

<i>Year of Production</i>	2010	2011	2012	2013	2014	2015	2016	2017	2018
<i>Technology Node</i>	hp45			hp32			hp22		
<i>Chip Frequency (MHz)</i>									
<i>On-chip local clock</i>	15,079		20,065	22,980		33,403	39,683		53,207


Clock frequency doubles every 3 years

## ITRS 2013

<i>Year of Production</i>	2013	2015	2017	2019	2021	2023	2025	2028
<i>Logic Industry "Node Name" Label</i>	"16/14"	"10"	"7"	"5"	"3.5"	"2.5"	"1.8"	
<i>On-chip local clock MPU HP [at 4% CAGR]</i>	5.50	5.95	6.44	6.96	7.53	8.14	8.8	9.9

Clock frequency doubles every 15 years


# Trend of CPU Frequencies

 

Stagnation in single-core CPU clock frequency  
[Colin Gillespie, 2016]


# Timing Optimization Methods

## Gate Sizing

 

$$T_{\min} = 3 + 12 + 1 = 16$$

## Retiming

 

$$T_{\min} = 3 + 7 + 1 = 11$$

The limit in the traditional timing paradigm


- Delay imbalances between flip-flop stages degrade performance
- Flip-flops have clock-to-q delays and impose setup time.



# VirtualSync Concept

fast path must be delayed

loop must be blocked

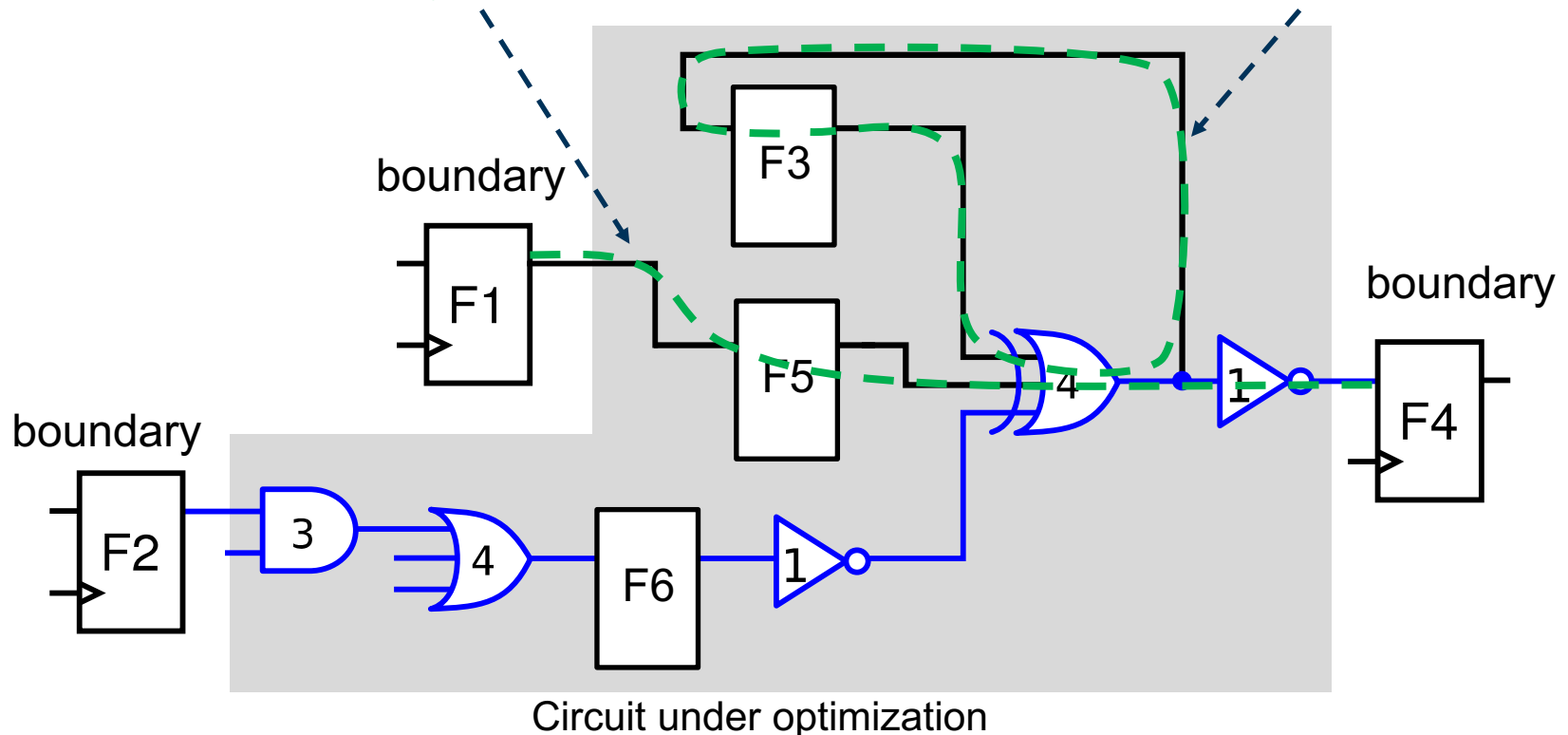


Step 1: Remove all flip-flops except those at the boundary of the module

Step 2: Block fast signals for timing synchronization, including

- signals arriving at boundary flip-flops too early through fast paths
- signals traveling across combinational loops





# VirtualSync Concept

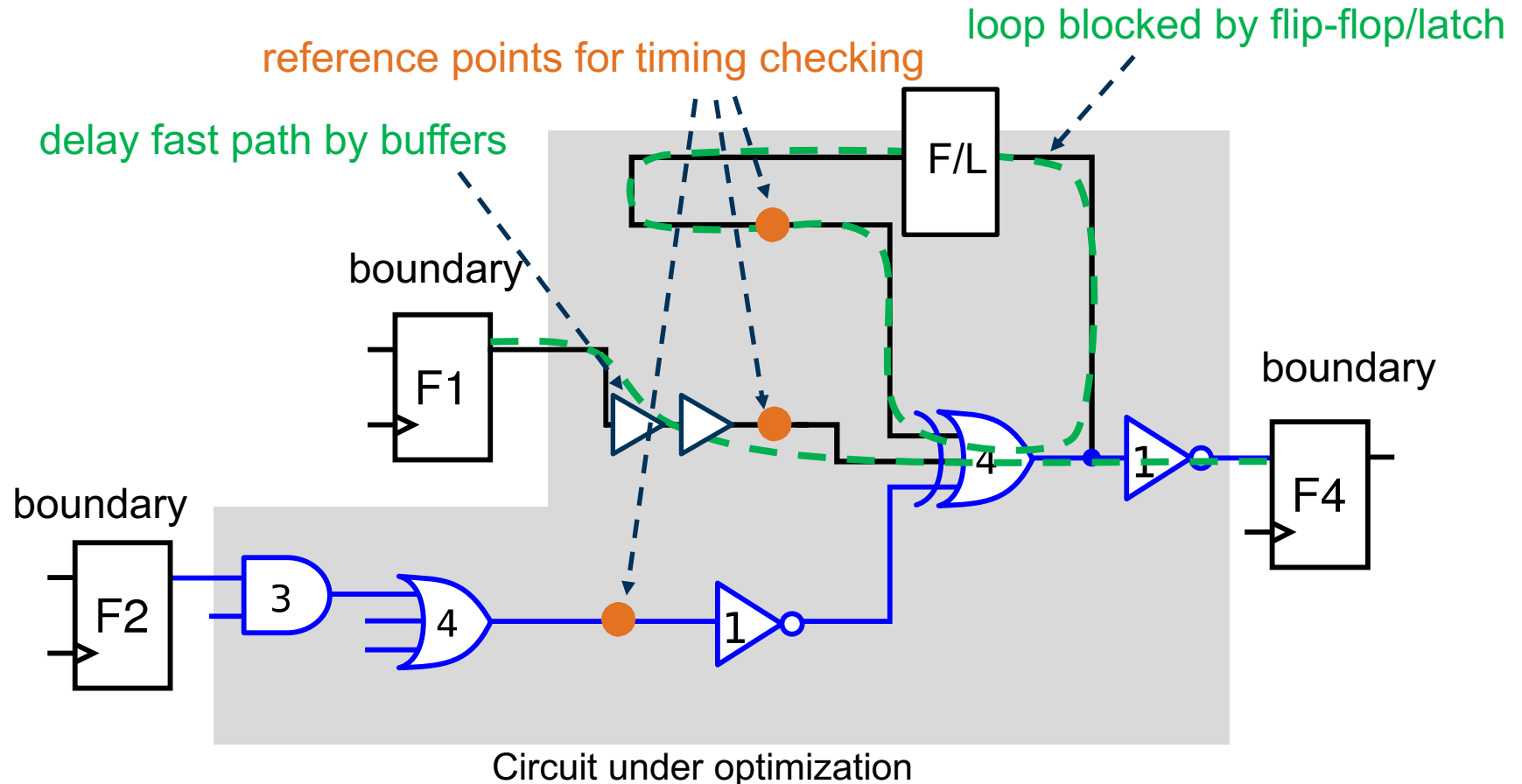



- **Delay units (logic gates, flip-flops and latches)** are used to slow down signals on fast paths and loops.
- **Reference points** provide relative timing information.

# Generalized Delay Units in VirtualSync

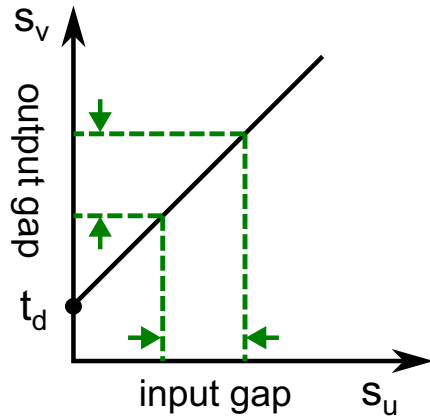 



(a)

  Linear delaying effect of a **combinational gate**



(b)

  Constant delaying effect of a **flip-flop**




(c) D: duty cycle

Piecewise delaying effect of a **latch**

Combinational gates, flip-flops and latches are considered as delay units only to slow down fast signals in VirtualSync.



# Results of VirtualSync

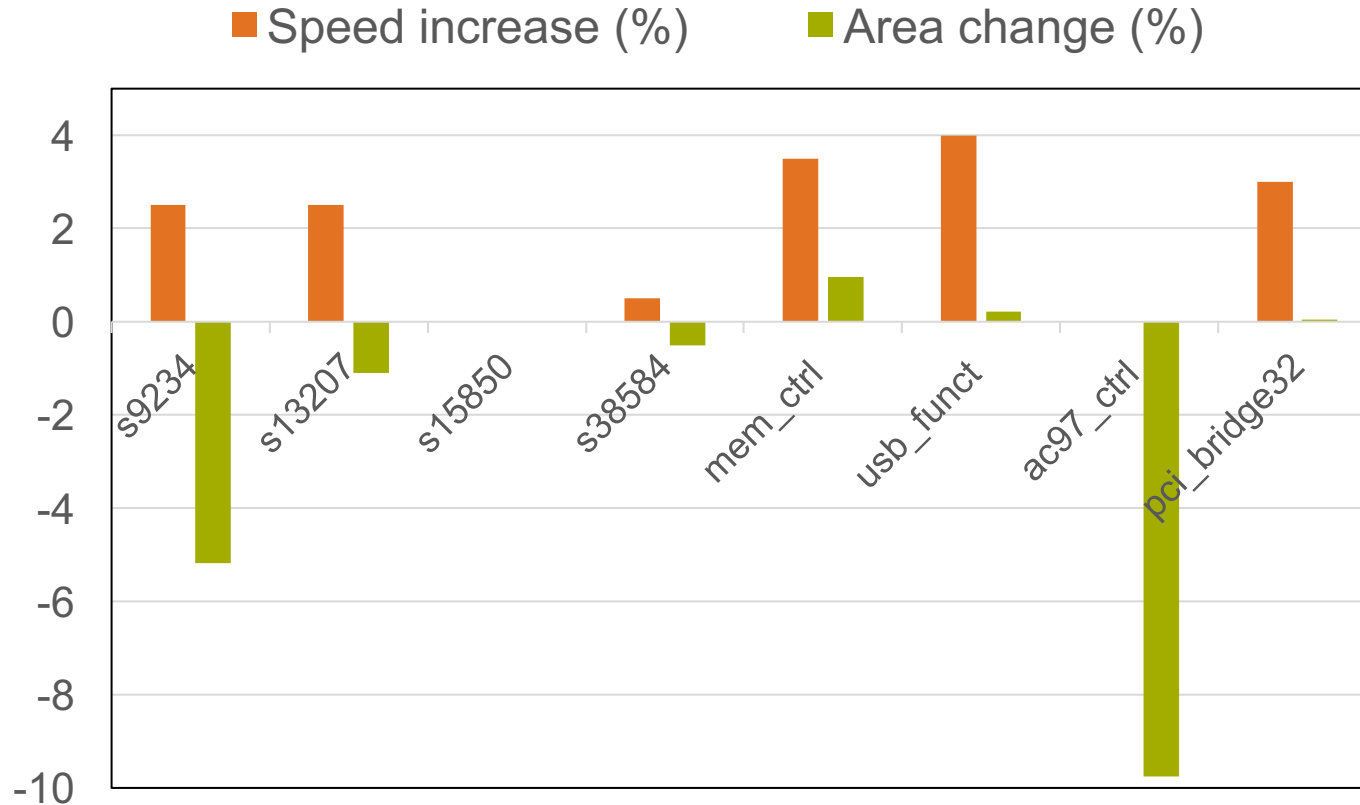

Performance increase and area change are compared with ideally balanced design.

 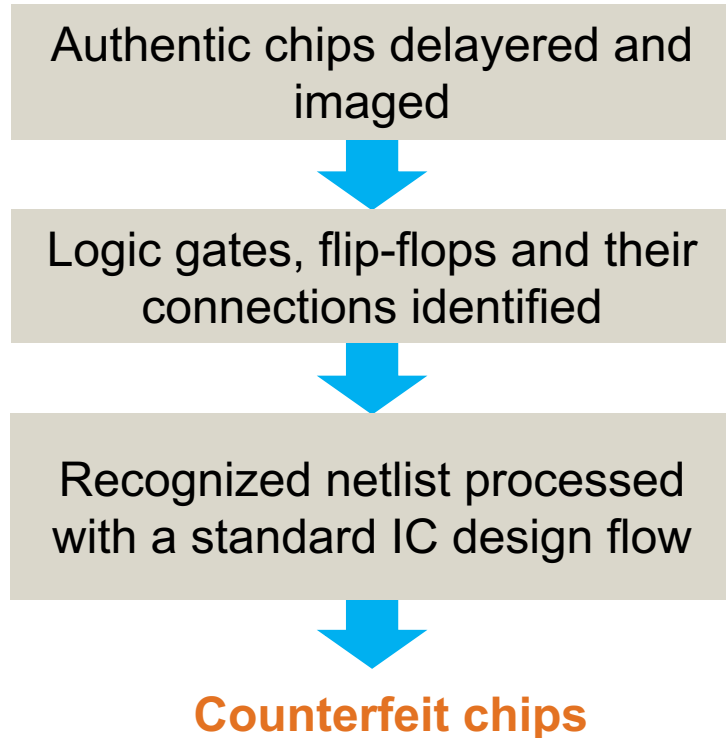
# Circuit Counterfeiting by Reverse Engineering

**Counterfeiting threat:** Illegal production of chips by a third party with a netlist recognized through reverse engineering




Optical and x-ray images of 64Gb Flash devices

# Counterfeiting with Traditional Timing

 

- Traditional timing model
  - All paths defined with respect to one clock period
  - Setup and hold time constraints satisfied between pairs of flip-flops
- A netlist is sufficient to reproduce a circuit using a standard EDA flow.

# Anti-Counterfeiting with VirtualSync

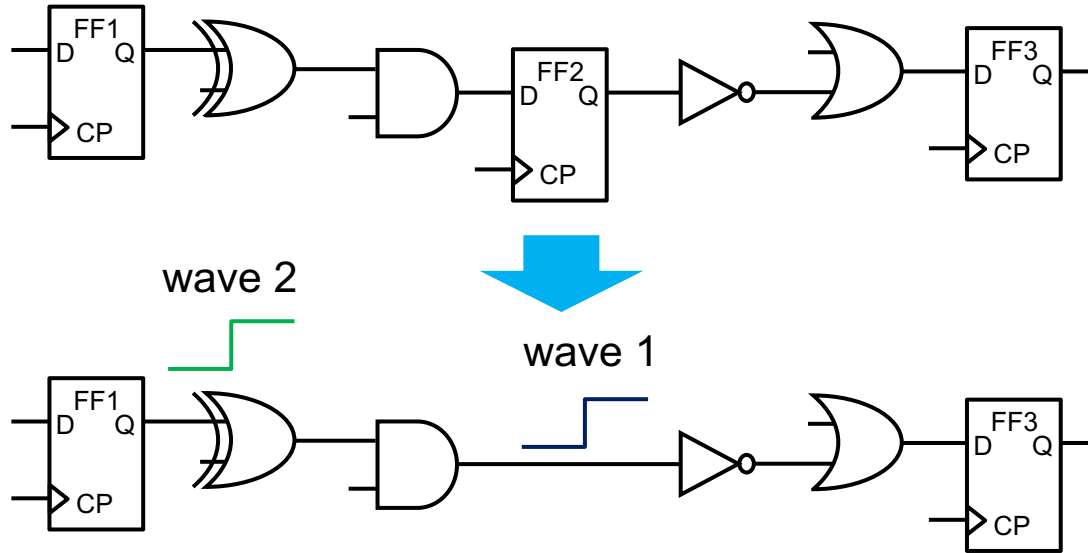

Timing camouflaged netlist

one logic wave

two logic waves

Recognized circuit loses synchronization

Additional effort to extract timing information

# Summary

- Virtual synchronization with generalized delay units demonstrates a good potential for high-performance designs.
- Timing camouflage opens up a new dimension of circuit netlist security.
- Exploration of design methodologies may improve circuit performance further and benefit interdisciplinary topics such as hardware security.

**Thank you for your attention!**